### How does a wye versus a delta power supply work?

For the same load, the current in the line and the power consumption are smaller (one third, to be more specific) if the load is connected in wye rather than delta. By the same token, a generator can deliver more power if the windings are delta connected.

### What is a wye connection?

First, points R, S, and T, which are the free ends of the load (winding) are connected to A?, B?, and C?. This makes a wye connection, but if R, S, and T are connected to A, B, and C (i.e., what is done after a further turning of the switch), then the load is delta connected to the three-phase line.

What is a wye-connected three-phase transformer?

A wye-connected three-phase transformer supplies power to a delta-connected induction motor. The transformer secondary has a phase voltage of 277 V and motor windings have a total impedance of 8 O. The motor operates with a power factor of 0.8. A wye-connected three-phase transformer supplies power to a delta-connected induction motor.

Why do three-phase loads form a balanced load?

Because the three separate sets of loads are identical and are simultaneously connected to electricity, they are balanced. Thus, all three-phase loads automatically form a balanced load for a three-phase circuit. Dealing with three-phase loads is much simpler than if independent single-phase loads are connected to a three-phase circuit.

Why do three-phase loads resemble single-phase systems?

In fact, many of the relationships and calculations for three-phase loads resemble their counterparts for single-phase systems. This is because the individual parts of the loads on the three phases behave alike. For instance, in a load consisting of resistors and inductors, there is a phase difference between the current and the voltage.

The total power measured in a three-phase system feeding a balanced wye-connected load is 10 kW at a power factor of 0.6 leading. If the line voltage is 400 V, calculate the line current IL ? Your Answer: Answer units

**SOLAR**°

The total power measured in a three-phase system feeding a balanced wye-connected load is 12 kW at a power factor of 0.6 leading. If the line voltage is 460 V, calculate the line current I L . There's just one step to solve this.



Question: A 3-phase power system consists of a wye-connected generatorconnected to the following loads, which are in parallel, through atransmission line. Load#1: Wye-connected load that consumes a total3-phase power of 3.6 kW at 0.8 power factor lag, when the generatorvoltage is set so that the voltage at the load is 480 V(line-to-line).



Web: https://www.gebroedersducaat.nl

SUPPORT REAL-TIME ONLINE DNITORING OF SYSTEM STATUS

~~

# CHEGG LOAD POWER OF A WYE SYSTEM

A three-phase load is a set of three exactly similar combinations of electric components arranged in exactly the same way (in series, parallel or other). The reason to have three-phase loads is the higher power demand.



A balanced, three-phase, wye-connected system has three identical phase impedances. The line-to-line volt- age is 240 V. The line-to-neutral current is 41 A. The power factor is 0.8 leading. Most nearly, the total appa- rent power in the system is (A) 7.9 kW - 35.9 kVA (B) 7.9 kW + 35.9 kVA (C) 14kW - 10 kVA (D) 14 kW + 10 kVA

The total power measured in a three-phase system feeding a balanced wye-connected load is 12 kW at a power factor of 0.6 leading. If the line voltage is 440 V, calculate the line current I, and the load impedance Zy.



Question: A three phase power system consists of wye-connected generator connected to a DELTA-connected load through a transmission line having an impedance Zline=1.9 248? ohms per-phase. The load impedance is ???

In a balanced three-phase wye-wye system, the total power loss in the lines is 400 W. v\_AN = 105.28/31.56degree V rms and the power factor of the load is 0.77 lagging. If the line impedance is 2 +

j1 ohm, determine the load impedance.

Question: A three-phase power system consists of a wye-connected generator connected to a delta-connected load through a transmission line having impedance of ?bar (Z)d=0.5?75??(C). ?>>?referenceCalculate:1.a. ?>>?The value (rms) ?>>?of the line-to-line currents IaA,IbB,Icc. (10 ?>>?points)1.b. ?>>?The value (rms) ?>>?of the voltage Uan, Ubn, Ucn.

4/11









A 3 phase Wye system with phase voltages of 81 V drives a balanced Wye load. The load is 67 < 3 0 ??? ohms per phase. What is the total Reactive Power in VAR? (Round the answer to 2 decimal places). (No sign required)

Question: 5. A three-phase power system consists of a wye-connected generator connected to a wye-connected load through a transmission line having an impedance of 1.5Ohms angle 75 degrees per phase. The load impedance is ???



You just need to do a comparison for the worst-case current peak. R im Vs(t) t=0 Fig. 2 Suppose we have the same power system source model as Problem Two, but this time we are considering the effect of modeling load, as illustrated in Fig. 3. A three-phase resistive grounded-wye load is being fed which consumes 6 MW.





DIESE

DIESEL �

A three-phase power system consists of a wye-connected ideal generator con- nected to a wye-connected load through a three-phase feeder The load has an impedance ZLL8 20L300 n/phase, and the feeder has an impedance 2s 1.545 n/phase.

Question: VAN E11.6 In a balanced three-phase wye-wye system, the total power in the lines is 650 W. V = 117/15? V rms and the power factor of the load is 0.88 leading. If the line impedance is 1 + j2 A, determine the load impedance.







5. A three-phase power system consists of a wye-connected generator connected to a wye-connected load through a transmission line having an impedance of 1.5 Ohms phase. The voltage at the load is 4,160 volts (line to line). Find a) the total complex power (3-phase) supplied by the generator b) The reactive power nendad s.. Jwer factor

**SOLAR**°

a three-phase power system consists of a wye-connected ideal generator connected to a wye\_connected load through a three-phase feeder. The load has an impedence Z L = 20 30 ohms/phase and the feeder has an impedence Z fdr = 1.5 75 ohms/phase. the terminal voltage of the load is 4.16 kV. Determine the terminal voltage of the generator and the line current ???

A three-phase balanced wye-wye system has a line voltage of 208 V rms. The line current is 12 A rms and the total real power absorbed by the load is 1700 W. Determine the load impedance per phase if the line impedance is negligible. Assume a lagging power factor. Zload 2

7/11





SUPPORT REAL-TIME ONLINE

~~





Question: "11.6 In a balanced three-phase wye-wye system, the total power in the lines is 650 W. an = 117/15? V rms and the power factor of the load is 0.88 leading. If the line impedance is + 12 1, determine the load impedance. ANSWER: 2 = 7???13.78.



Question: 5. A three-phase power system consists of a wye-connected generator connected to a wye-connected load through a transmission line having an impedance of 1.5Ohms phase. The voltage at the load is 4,160 volts (line to line). Find a) the total complex power (3-phase) supplied by the generator b) The reactive power nendad s.. Jwer factor



Question: a three phase power system consists of a wye connected source a wye connected load through a transmission has an apparent powe S =3+j4 Kva and a power factor of 0.6 lagging determine the reactive power produced by the capacitor bank required to correct the power factor to PF=0.9 lagging power systems



Question: 1. A 3 phase Wye system with phase voltages of 90 V drives a balanced load. The Wye load is 85<45? ohms per phase. a. What is the total Apparent Power in VA? b. What is the total True/Real Power in W? c. What is the total reactive power in ???

Question: 8.) The line voltage of a 3-phase wye connected power system is 480V. If a 3-phase delta connected resistive load is connected to the power system answer the following: [12 points] a) What is the voltage across each resistor? b) If R1 = 8.5 ohms (per phase), what is the current in each line (line current)?

In a three-phase balanced system an abc-sequence wye-connected source with Van = 220 20? V rms supplies power to a wye-connected load that consumes 36 kW of power in each phase at a pf of 0.75 lagging. Three capacitors, each with an impedance of -j2.092 are connected in parallel with the original load in a wye configuration. Determine the







In a balanced three-phase wye-wye system, the total power loss in the lines is 530 W. VAN load is 0.88 lagging. If the line impedance is 4 +j1 ?(C), determine the load impedance 105.28???31.65? V rms and the power factor of the (a) Find the real part of the load impedance. (b) Find the imaginary part of the load impedance



The total power measured in a three-phase system feeding a balanced wye-connected load is 12 kW at a power factor of 0.6 leading. If the line voltage is 440 V, calculate the line current I and the load impedance Zy. =  $e''02 \cos(0)+2e0\sin(0) + er0? \sin(0)$ (0) ar00 (iii) u e sin 0; 1 (iv) z=uv-w:



Question 2 A 3 phase Wye system has line currents of: Phase A: 6<[0] A Phase B: 6<[-120]?A Phase C: 6<[120] A What is the neutral current value? the result is for the magnitude value only. Question 3 A 3 phase Wye system with phase voltages of 96 V drives a balanced load. The Wye load is 109<60? ohms per phase.



The magnitude of the complex power (apparent power) supplied by a three-phase balanced wye-wye system is 3600 VA. The line voltage is 208 v rms. If the line impedance is negligible and the power factor angle of the load is 75?, determine the load impedance.

A three-phase power system consists of a wye-connected generator connected to a wye connected load through a transmission line having a per-phase impedance magnitude of 2.5 Ohms and angle 65 degrees. The load consumes a total three-phase apparent power of 450 kV A at 0.8 power factor lag when the generator voltage is set so that the voltage at



Determine the line voltage, load phase voltage, generator phase current, line current, load phase current and the total power delivered to the load. This is a homogenous (Y-Y) system, therefore the load phase voltage and ???

